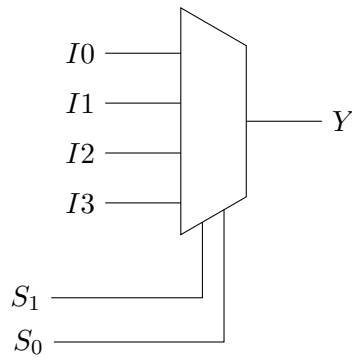


Homework 10  
Andrei Tumbar

April 15, 2020

- 1 Write VHDL code (dataflow) to describe the circuit in two ways.

2 Design a multiplexor circuit to describe the VHDL code.



3 Design a 3:8 decoder circuit to describe the VHDL code.

